

ECE601 | Advanced Analog Integrated Circuits

Assignment No. 2

Abdelrahman Hassan Muhammed – Student ID : 202211466

Design amplifier using inductors/capacitors from design kit that achieve $GT > 9\text{dB}$ at 12GHz including matching network. Use kit inductors/capacitors to match transistor input and output impedance to $50\ \Omega$, make sure your design is unconditionally stable. Plot GT , G_p , G_a , S_{21} , S_{12} , S_{11} , S_{22} , NF , k factor versus frequency. You can choose number of fingers=10

Design procedures



Step 1 (Choosing topology) : a basic common source stage with two modifications

A - Inductive degeneration : used to tune input matching to get the real part of the input impedance equal to $50\ \Omega$ directly and for the remaining imaginary part a single inductor is added in series to cancel it which simplifies the input matching network a lot. Also, this inductive degeneration helps in improving stability of the amplifier.


B - Cascode Transistor is added to isolate the output from the input and also to increase the gain that can be obtained from the amplifier.

Step 2 (Matching the Input) : A series inductor at the gate used to cancel the imaginary part of the Z_{in} and another one at the tune the real part to get the $50\ \Omega$

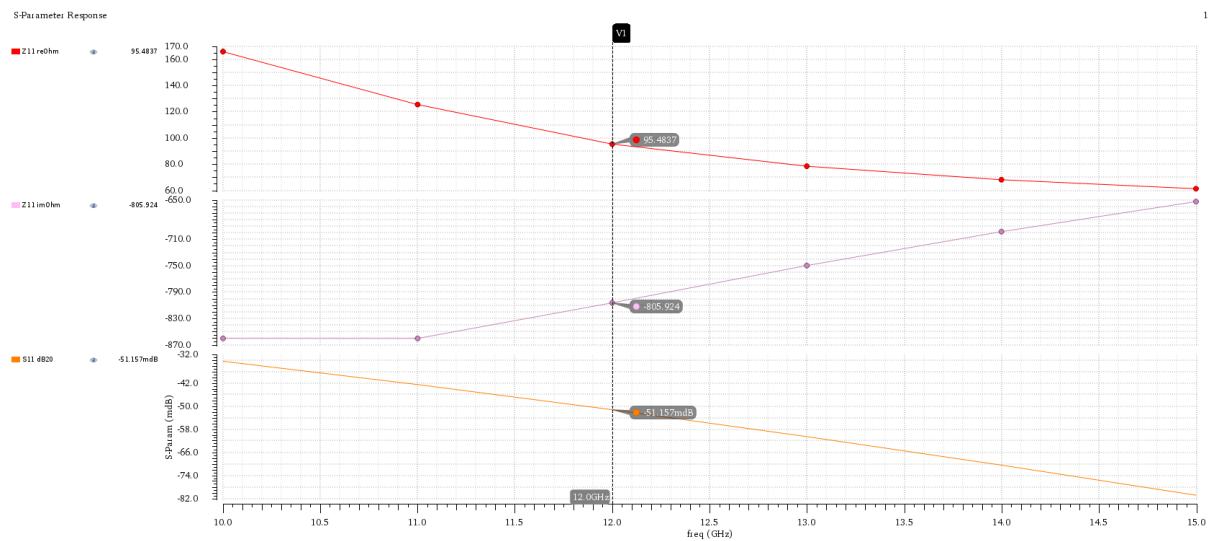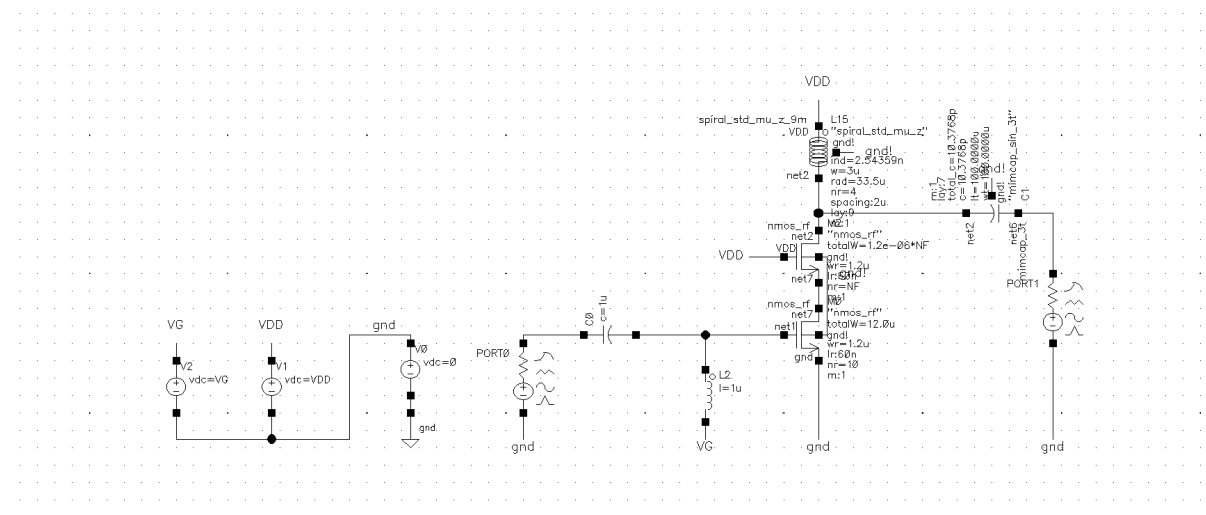
A – The circuit input impedance with no matching at the input



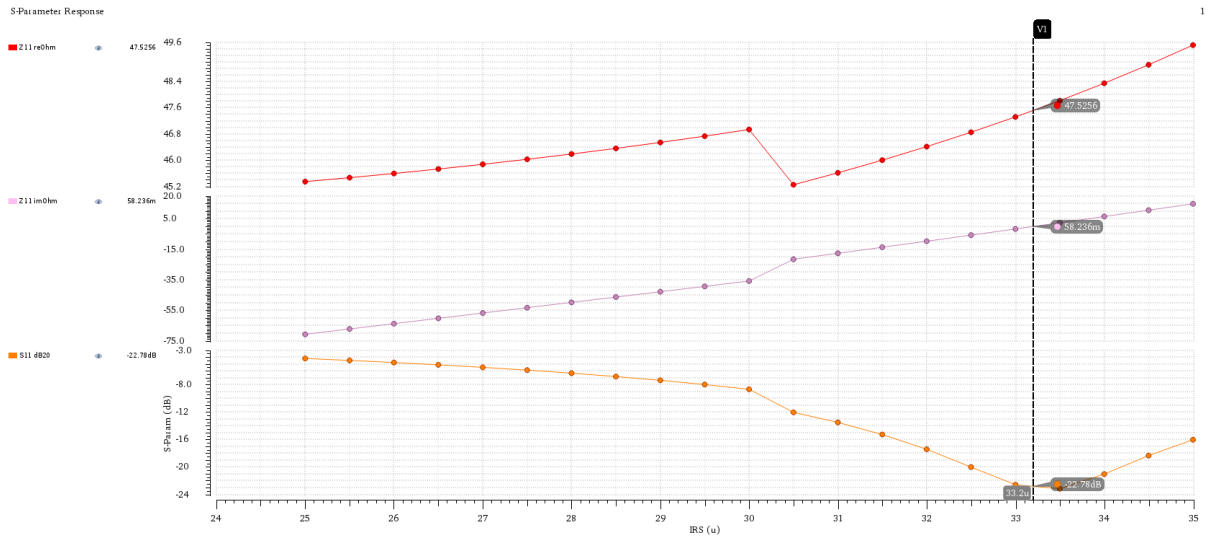B – The maximum value of one inductor of the kit is not enough to cancel the imaginary part of Z_{in} so I use two inductors in series and tune the L needed by changing the inner radius of the inductor




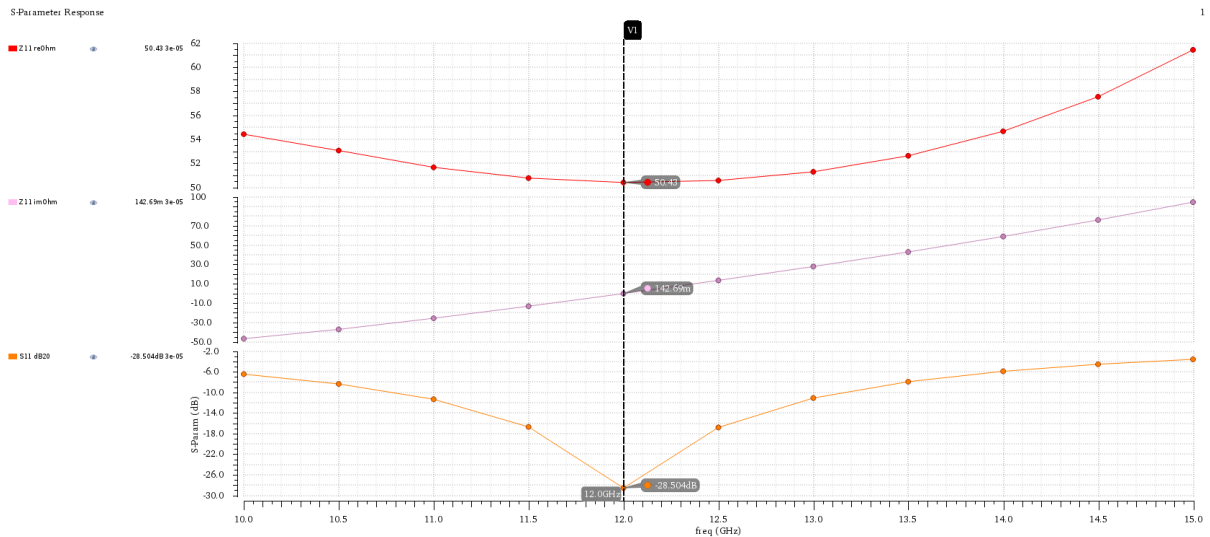C – The real part of Z_{in} achieved by the inductor at the source




Step 3 (Matching the output) : An output matching network is added to match the output impedance to 50Ω . This network is an L matching network for simplicity.

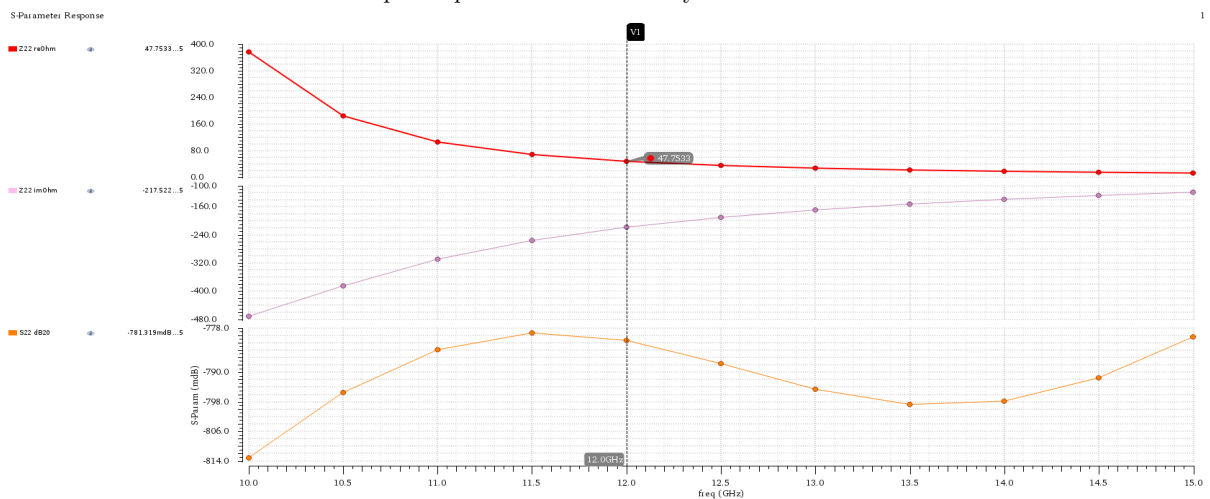A – First we check the output impedance with arbitrary L and C for the network




B – Ga, Gp, Gt

S-Parameter Response

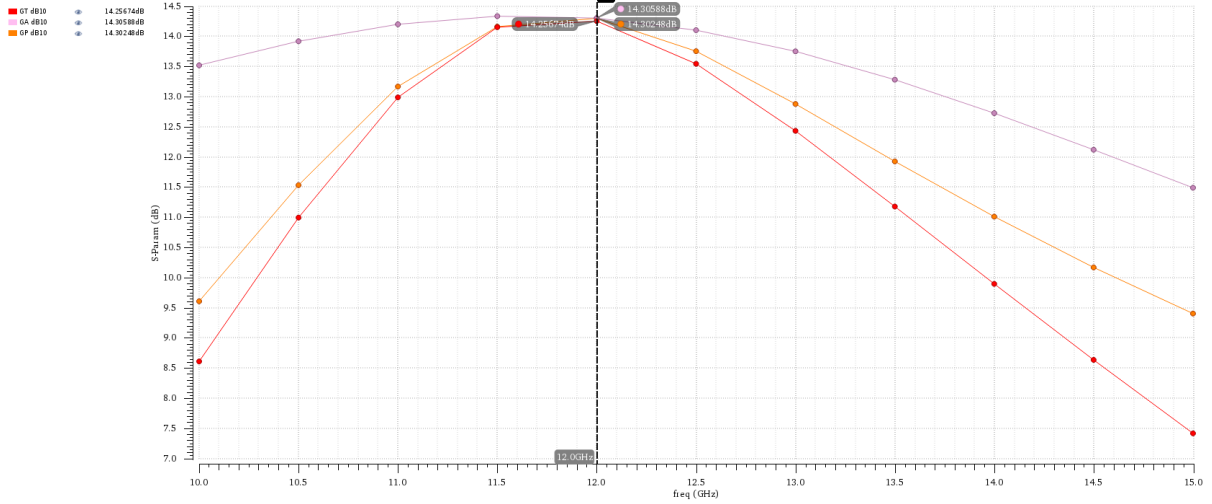


C – S11 and Input Impedance

S-Parameter Response

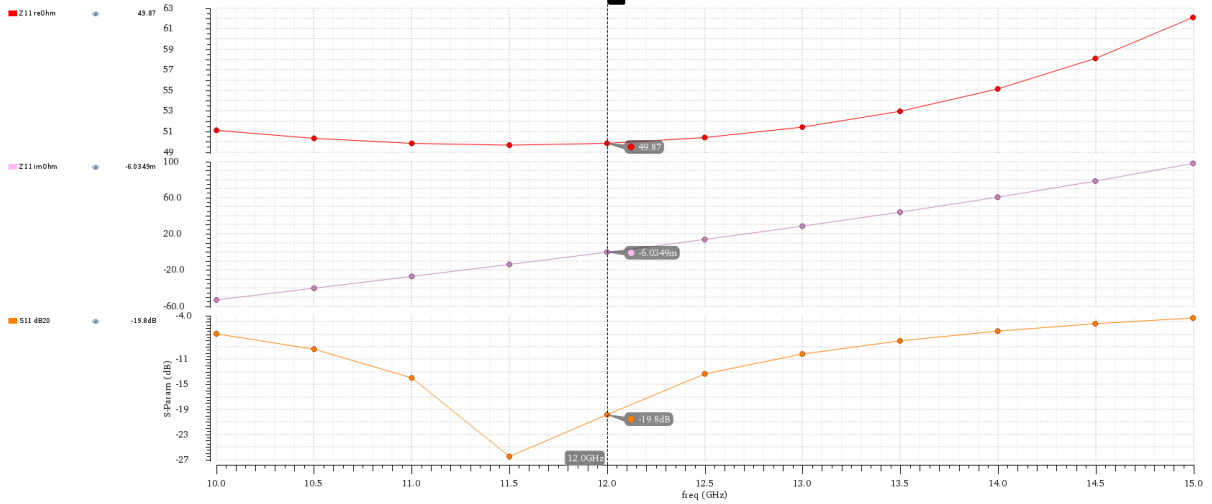


D – S22 and Output Impedance


S-Parameter Response

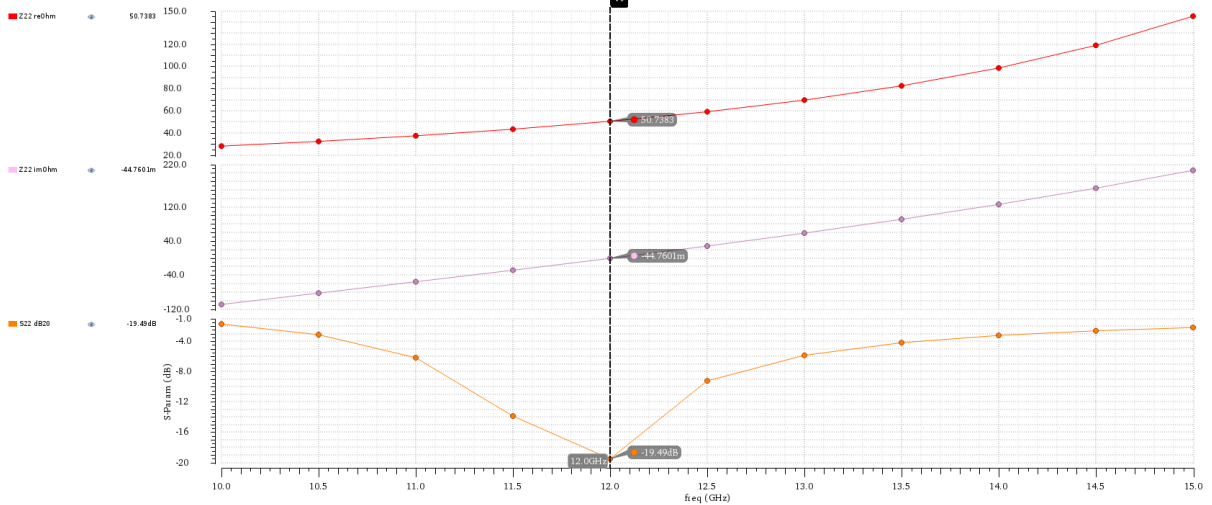


E – S21 and S12

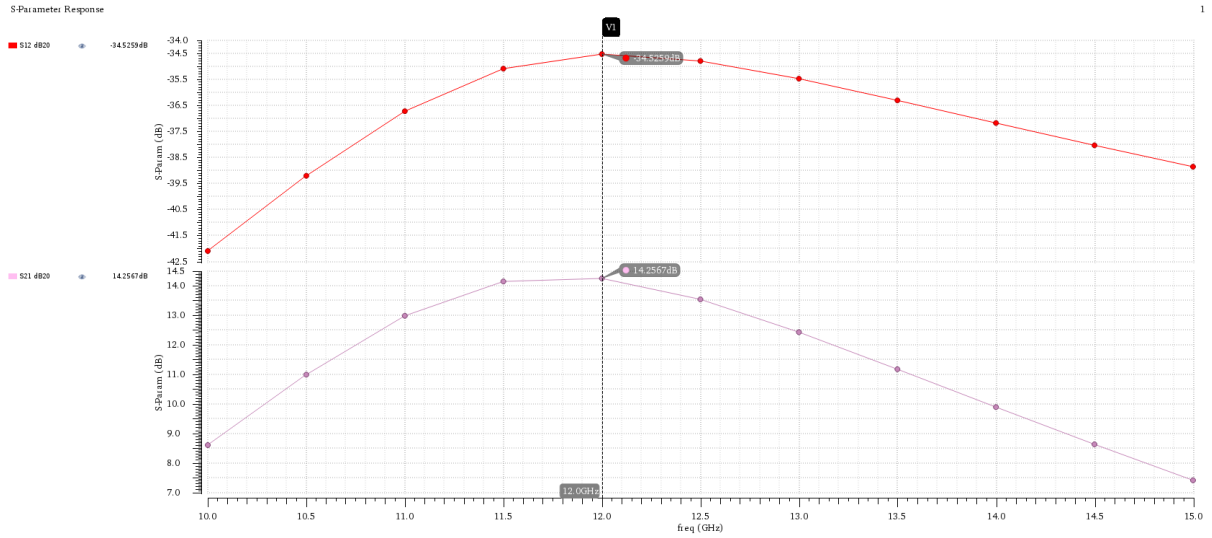

F – Noise Factor

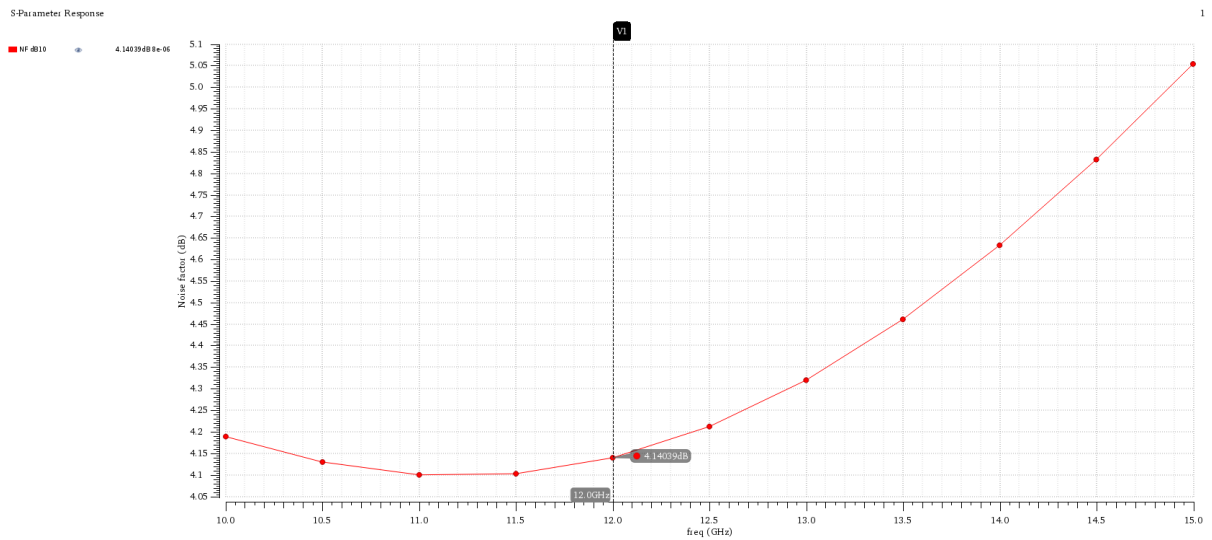

G – K and delta factors

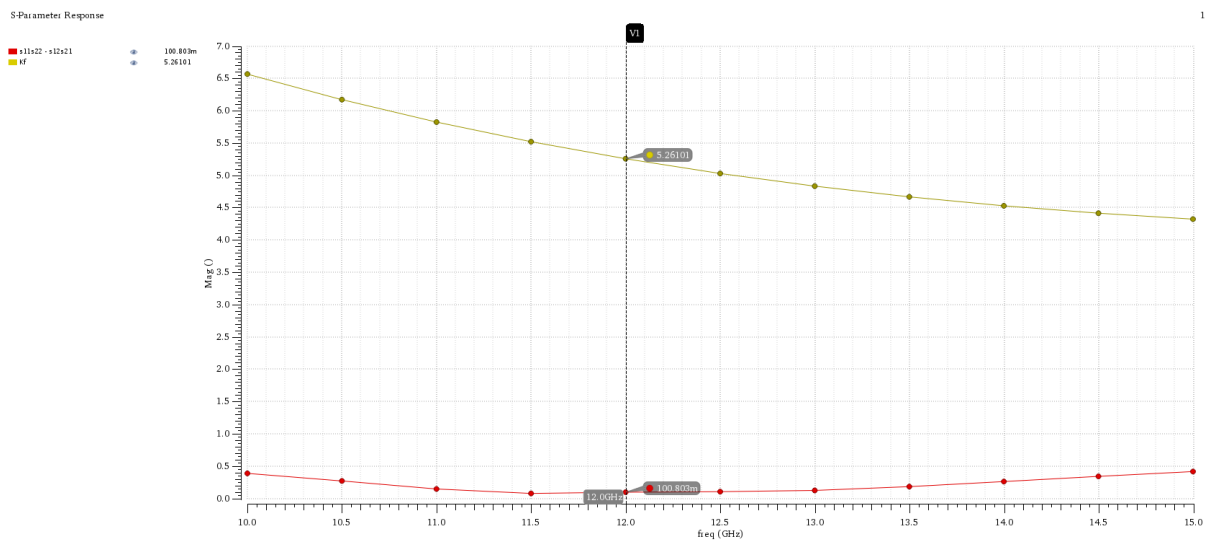

The K factor > 1 and the delta is $< 1 \rightarrow$ So the design is unconditionally stable